


- 7) a) Interface D/A & A/D converters with 8051 & explain in detail.

Digital to Analog (DAC) converters:

The digital inputs are converted to current I_{ans} and by connecting resistors the I_{out} in we can convert the result to voltage. The total current I_{out} is a function of the binary numbers at the $D_0 - D_7$ inputs of the DAC0808 and the reference current I_{ref} . and is as follows

$$I_{out} = I_{ref} \left(\frac{D_7}{2} + \frac{D_6}{4} + \frac{D_5}{8} + \frac{D_4}{16} + \frac{D_3}{32} + \frac{D_2}{64} + \frac{D_1}{128} + \frac{D_0}{256} \right)$$

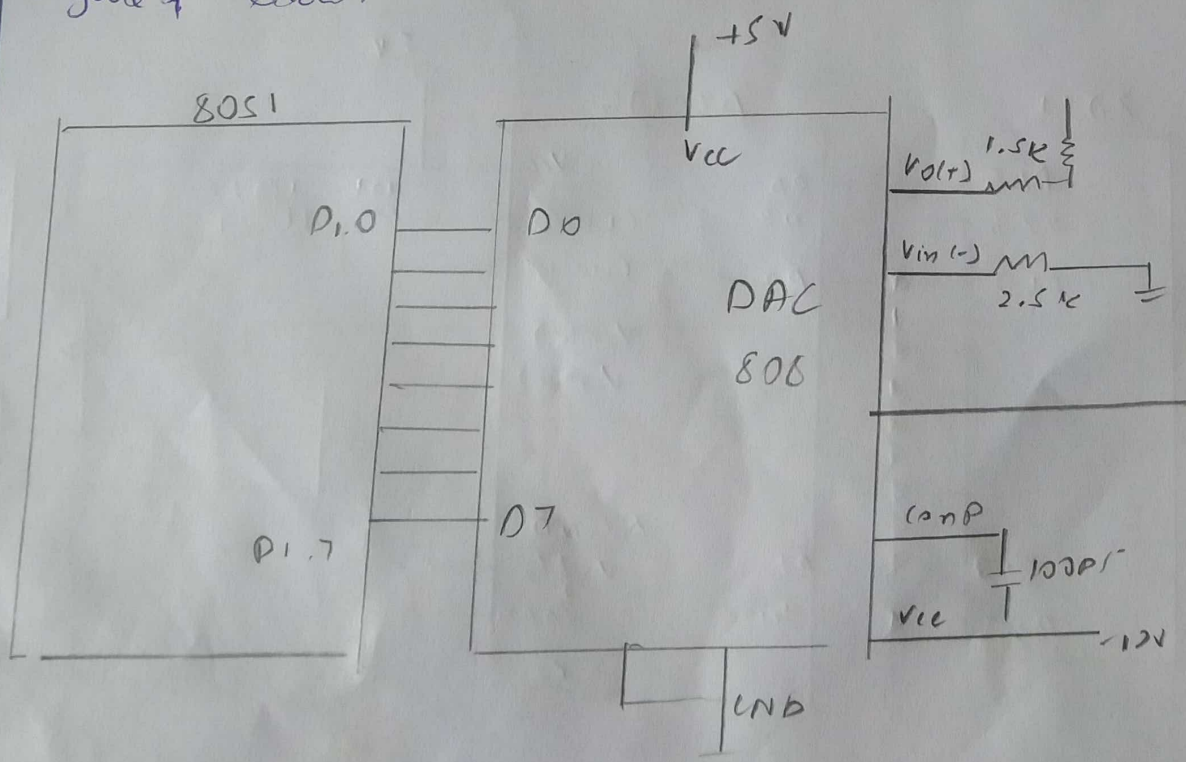Usually reference current is $2mA$. Ideally we connect the output I_{out} to a resistor, convert this current to voltage, and monitor the output on the scope. But this can cause inaccuracy, hence an opamp is used to convert the output current to voltage. The 8051 connected to DAC 0808 is as shown in the figure below.





Analog to digital converter:

The following steps must be followed for data conversion by the ADC 809 chip

1. Make $CS = 0$ and send a 1 to 4 pulse to \overline{WR} to start conversion
2. Monitor the \overline{INTP} pin, if high keep polling, but if low, conversion is complete, go to next step.
3. Make $CS = 0$ and send 4 to 1 pulse to pin \overline{RD} to get the data out

Figure shows the read and write timing for ADC-809.

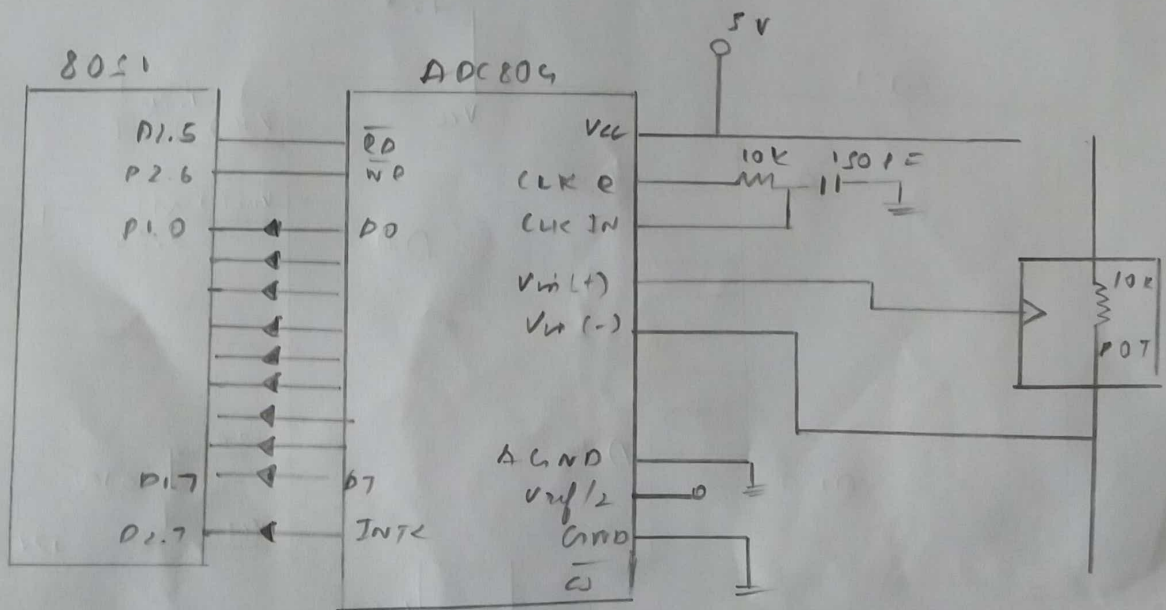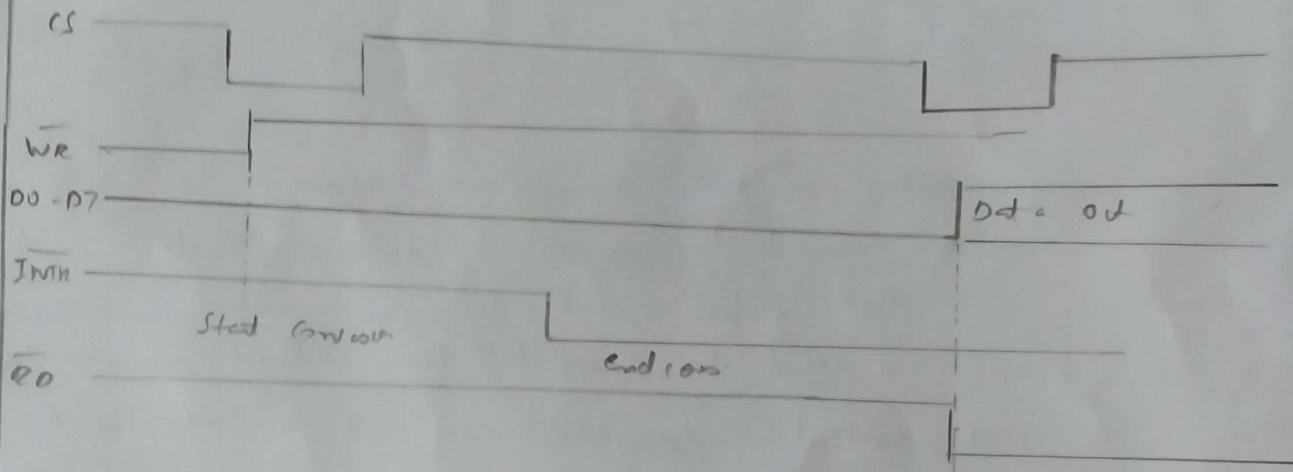

Stepper Motor Interface:

Stepper motor has a magnet rotor called as stator which is surrounded by stator. The stator has a magnet field in the clockwise direction. The coils are commonly connected to ground or +5V. The other end is powered with a fixed sequence such that the motor rotates in a particular direction.

Step angle:

Step angle is defined as the minimum degree of rotation of a single step.

$$\text{No of steps per revolution} = 360^\circ / \text{step angle}$$

$$\text{Steps per second} = (\text{rpm} \times \text{steps per revolution}) / 60$$

Example: step angle = 2°
 No of steps per revolution = 180

Switching Sequence of Motor:

As discussed earlier the coils need to be energized for the motor to rotate. This can be done by sending a step sequence to one end of the coil while the other end is commonly connected to ground. The step sequence sent out can make it a one phase or a two phase. In full step sequence, it can be a combination of one and two phase ON for half step sequence. Both are tabulated below.

Full step

Two phase ON

clockwise	Step #	A	B	C	D	counterclockwise
	1	1	0	0	1	
	2	1	1	0	0	
	3	0	1	1	0	
	4	0	0	1	1	


One phase ON

Clockwise



Step #	A	B	C	D
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1

Count - down

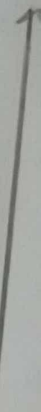


Half Step (8-sequence)

The sequence is tabulated below

Step #	A	B	C	D
1	1	0	0	1
2	1	0	0	0
3	1	1	0	0
4	0	1	0	0
5	0	1	1	0
6	0	0	1	0
7	0	0	1	1
8	0	0	0	1


8051 connected to stepper motor

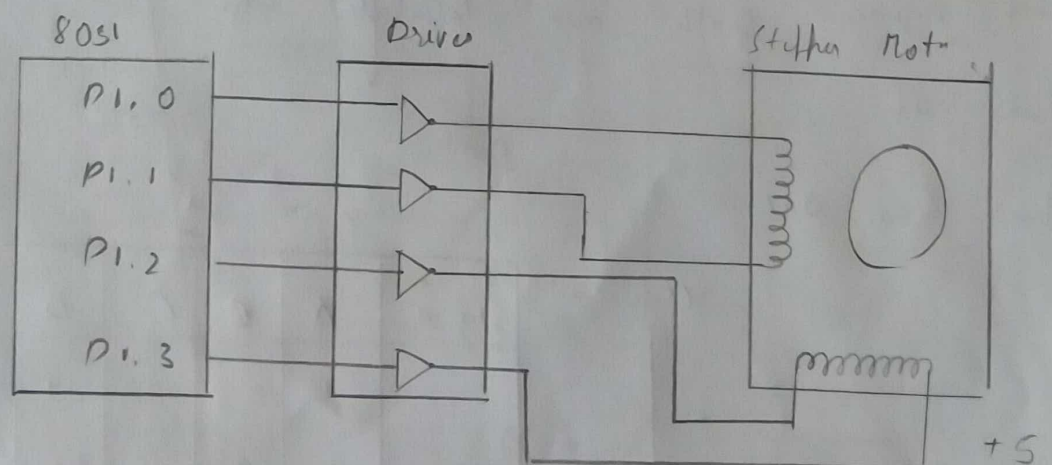

Explain neatly how you can interface 8051 LCD display! (3)


LCDs are widely used and preferred over LEDs (7 seg & multi-segment LEDs) due to the following reasons:

- The declining price of LEDs
 - The ability to display numbers, characters and graphics
 - Incorporation of a refreshing controller into the LED, thereby relieving the CPU of the task of refreshing the LED.
- In contrast, the LED must be refreshed by the CPU to keep displaying the data.
- Ad of program - for characters and graphics.
- This exercise is an intelligent LCD display of two lines, 20 characters per line, that is interfaced to the 8051.

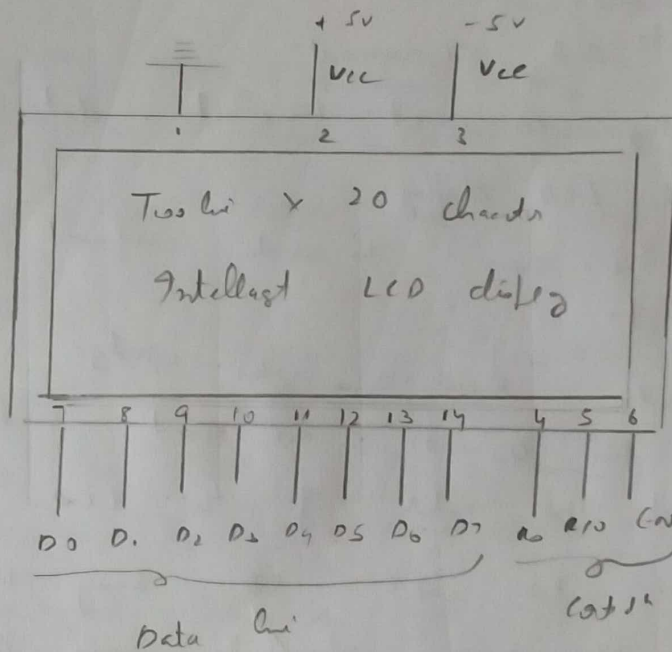

- The display contains two internal byte write registers, one for command (RS=0) & the second for characters to be displayed.
- It also contains a user-programmable RAM (the character RAM) that can be programmed to generate any desired character that can be stored as a dot matrix.
- Pin 1 is used to provide the common anode light & is connected to ground.

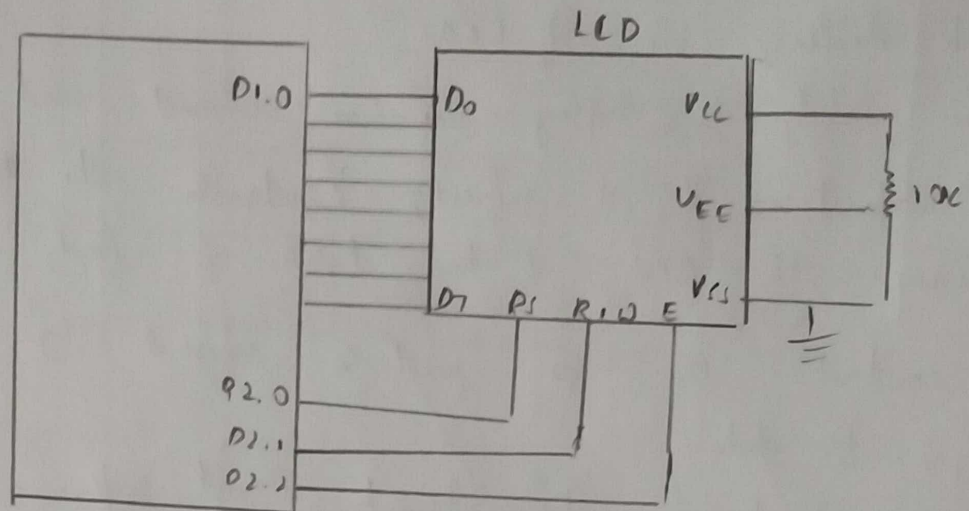- The display takes various amounts of time to accomplish the function.
- Usually LCD bit D7 is monitored for a logic '1' by the system to ensure the display is not overwritten.



LCD Connected to 8051

- If $RS=0$ the instruction command sent is clear code register is selected. Allowing the user to send a command.
- Send a clear display, cursor at home etc. data is treated as a command to the LCD display.
- R/W = 0 allows the user to write information to the LCD and read information from it.
- $R/W = 1$ when reading, $R/W = 0$ when writing.
- The 8-bit data bus D0-D7 is used to send data to the LCD or read the contents of the LCD memory.
- We also use $RS=0$ to check the busy flag bit to see if the LCD is ready to receive data. The busy flag is D7 and only send data when $R/W = 1$ and $RS = 0$ follows.
- If $R/W = 1$, $RS = 0$ when D7 = 1 the LCD is busy with its current operation and will not accept new data.

Interface External RAM & ROM to 8051 microcontroller

Interface external ROM with 8051:

- In 8051 port 0 provides 16 bit address to access the external memory.
- Port 0 is multiplexed address/data bus.
- By using ALE pin
 - ALE = 0 → data latch (Access data from ROM)
 - ALE = 1 → address latch (Access data address from ROM)
- O/P signal of 8051 must be connected to (\overline{PSEN}) the OE pin of ROM containing the program code.
- EA pin (active low)
 - 1 → Pgm is an chip to ROM
 - 0 → Pgm to be access from external memory
- \overline{PSEN} : 0 → can access external memory
1 → cannot access external memory
- Latch is a 8 bit latch used for address & data multiplexing
- External program memory access is possible when EA pin is low
- It is necessary to latch the low address byte when the external program byte is read on the data bus.
- The low address address byte is latched as the ALE pulse goes low.

